

P1.

Starting with the canonical sum-of-products for f get

$$\begin{aligned}
 f &= \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1x_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3 + x_1x_2x_3 \\
 &= x_1(\bar{x}_2\bar{x}_3 + \bar{x}_2x_3 + x_2\bar{x}_3 + x_2x_3) + x_2(\bar{x}_1\bar{x}_3 + \bar{x}_1x_3 + x_1\bar{x}_3 + x_1x_3) \\
 &\quad + x_3(\bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1\bar{x}_2 + x_1x_2) \\
 &= x_1(\bar{x}_2(\bar{x}_3 + x_3) + x_2(\bar{x}_3 + x_3)) + x_2(\bar{x}_1(\bar{x}_3 + x_3) + x_1(\bar{x}_3 + x_3)) \\
 &\quad + x_3(\bar{x}_1(\bar{x}_2 + x_2) + x_1(\bar{x}_2 + x_2)) \\
 &= x_1(\bar{x}_2 \cdot 1 + x_2 \cdot 1) + x_2(\bar{x}_1 \cdot 1 + x_1 \cdot 1) + x_3(\bar{x}_1 \cdot 1 + x_1 \cdot 1) \\
 &= x_1(\bar{x}_2 + x_2) + x_2(\bar{x}_1 + x_1) + x_3(\bar{x}_1 + x_1) \\
 &= x_1 \cdot 1 + x_2 \cdot 1 + x_3 \cdot 1 \\
 &= x_1 + x_2 + x_3
 \end{aligned}$$

P2.

Truth Tables a, b, c


X	Y	Z	a	A	B	C	b
0	0	0	0	0	0	0	1
0	0	1	0	0	0	1	1
0	1	0	0	0	1	0	0
0	1	1	1	0	1	1	1
1	0	0	0	1	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	1	0	0
1	1	1	1	1	1	1	1

- a) Sum of Minterms: $\bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ$
 Product of Maxterms: $(X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + Z)$
- b) Sum of Minterms: $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC$
 Product of Maxterms: $(A + \bar{B} + C)(\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$

P3.


P3. $f(x_1, x_2, x_3) = \sum m(3, 4, 6, 7)$

$$\begin{aligned}
 f &= x_1' x_2 x_3 + x_1 x_2' x_3' + x_1 x_2 x_3' + x_1 x_2 x_3 \\
 &= x_1' x_2 x_3 + x_1 x_2' x_3' + x_1 x_2 (x_3' + x_3) \\
 &= x_1' x_2 x_3 + x_1 x_2' x_3' + x_1 x_2 \\
 &= x_1' x_2 x_3 + x_1 (x_2' x_3' + x_2) \\
 &= x_1' x_2 x_3 + x_1 (x_2' + x_2) (x_3' + x_2) \\
 &= x_1' x_2 x_3 + x_1 x_3' + x_1 x_2 \\
 &= x_1' x_2 x_3 + x_1 x_2 + x_1 x_3' \\
 &= x_2 (x_1' x_3 + x_1) + x_1 x_3' \\
 &= x_2 (x_1' + x_1) (x_3 + x_1) + x_1 x_3' \\
 &= x_1 x_2 + x_2 x_3 + x_1 x_3'
 \end{aligned}$$

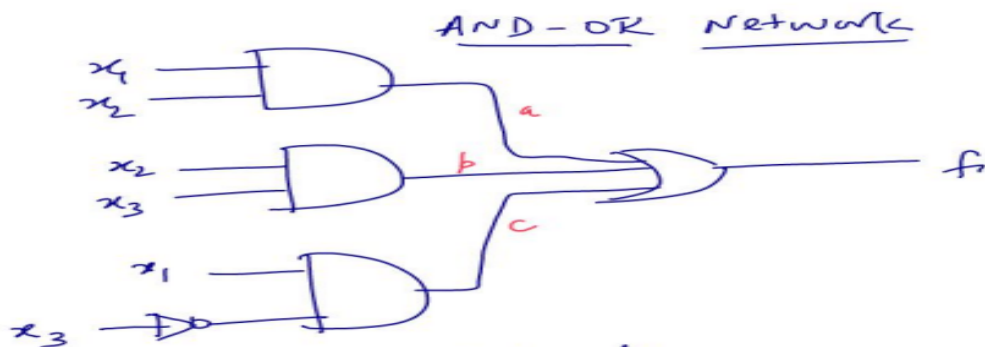


NAND only Network

(a) Double inversion on wires a, b, c

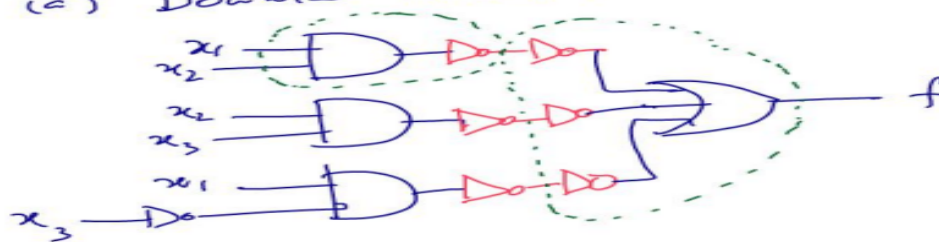

(b)
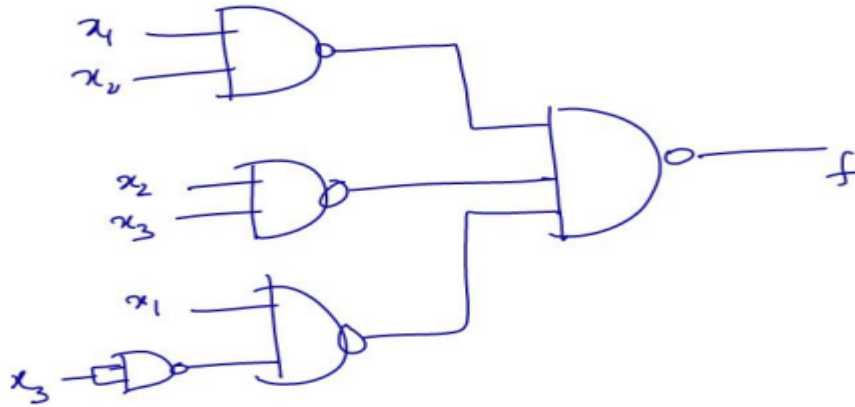
$$\begin{aligned}
 \text{NAND gate with double inversion on inputs} &= \text{AND gate} \\
 \text{NAND gate with double inversion on output} &= \text{OR gate}
 \end{aligned}$$



P4. a)

(a) Min terms

$$M(X, Y, Z) = \sum m(3, 5, 6, 7) = \bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ$$

$$N(X, Y, Z) = \sum m(1, 2, 4, 7) = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$


Max terms

$$M(X, Y, Z) = \prod M(0, 1, 2, 4) = (X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + Z)(\bar{X} + Y + Z)$$

$$N(X, Y, Z) = \prod M(0, 3, 5, 6) = (X + Y + Z)(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)$$

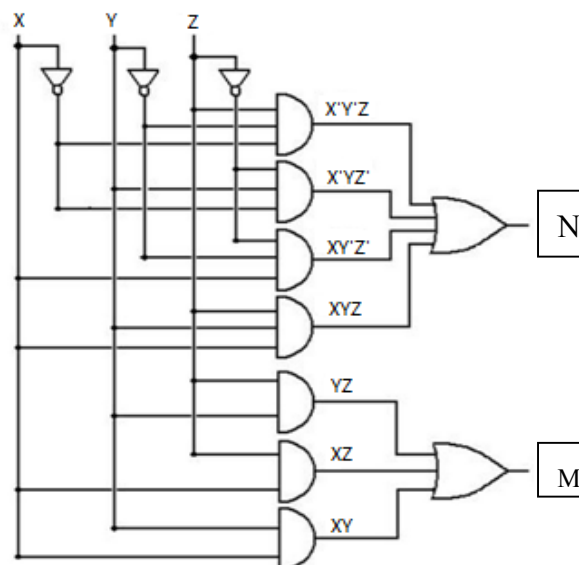b) $M = YZ + XZ + XY$,

$$N = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$



P5.

x 1	x 2	y 1	y 2	X=x1x2	Y=y1y2	F
0	0	0	0	$(00)_2=(0)_{10}$	$(00)_2=(0)_{10}$	1
0	0	0	1	00=0	01=1	0
0	0	1	0	00=0	10=2	0
0	0	1	1	00=0	11=3	0
0	1	0	0	01=1	00=0	0
0	1	0	1	01=1	01=1	1
0	1	1	0	01=1	10=2	0
0	1	1	1	01=1	11=3	0
1	0	0	0	10=2	00=0	0
1	0	0	1	10=2	01=1	0
1	0	1	0	10=2	10=2	1
1	0	1	1	10=2	11=3	0
1	1	0	0	11=3	00=0	0
1	1	0	1	11=3	01=1	0
1	1	1	0	11=3	10=2	0
1	1	1	1	11=3	11=3	1

$$\text{SOP} = x_1'x_2'y_1'y_2' + x_1'x_2y_1'y_2 + x_1x_2'y_1y_2' + x_1x_2y_1y_2$$

$$\begin{aligned} \text{POS} = & (x_1+x_2+y_1+y_2')(x_1+x_2+y_1'+y_2)(x_1+x_2+y_1'+y_2')(x_1+x_2'+y_1+y_2) \\ & (x_1+x_2'+y_1'+y_2)(x_1+x_2'+y_1'+y_2')(x_1'+x_2+y_1+y_2)(x_1'+x_2+y_1+y_2') \\ & (x_1'+x_2+y_1'+y_2')(x_1'+x_2'+y_1+y_2)(x_1'+x_2'+y_1+y_2')(x_1'+x_2'+y_1'+y_2) \end{aligned}$$

P6.

(a) The NAND function $F = (A.B)'$ If we set $B=1$, then $F = (A.1)' = A'$.

In other words, we can implement the NOT function by connecting one of the inputs of a 2-input NAND gate to 1 (Vdd).

(b) The NOR function $F = (A+B)'$ If we set $B=0$, then $F = (A+0)' = A'$.

In other words, we can implement the NOT function by connecting one of the inputs of a 2-input NOR gate to 0 (Gnd).

(c) The 2-1 MUX function $F = S'.x_0 + S.x_1$ If we set $x_0=1$ and $x_1=0$, then $F = S'.1 + S.0 = S'$.In other words, we can implement the NOT function by connecting the x_0 input of a 2-1 MUX to 1 (Vdd), the x_1 input to 0 (Gnd), and the signal to be inverted to S.

P7.

