

Cpr E 281 HW07 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Arithmetic Circuits and Combinational-Circuit Building Blocks Assigned Date: Eighth Week Due Date: First class of 9th week

P1. (6 points) Negate the following binary numbers in 4-bit 2's complement representation:

(Remark: Negate means you find the negative of the number.)

(a) 0001; (b) 1100; (c) 0111

To negate any number in 2's complement, flip all the bits and then add 1.

(a) $1110+1 = 1111$

(b) $0011+1 = 0100$

(c) $1000+1 = 1001$

P2.

Construct the truth table

x_{n-1}	y_{n-1}	c_{n-1}	c_n	s_{n-1} (sign bit)	Overflow
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

Note that overflow cannot occur when two numbers with opposite signs are added. From the truth table overflow expression is

$$Overflow = \bar{c}_n c_{n-1} + c_n \bar{c}_{n-1} = c_n \oplus c_{n-1}$$

P3. (6 points) Give the 4-bit 2's complement representation for the following decimal numbers:

(a) -6; (b) -1; (c) 6

(a) $-6 = 1010_2$

(b) $-1 = 1111_2$


(c) $6 = 0110_2$

Cpr E 281 HW07 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Arithmetic Circuits and Combinational-Circuit Building Blocks Assigned Date: Eighth Week Due Date: First class of 9th week

P4.

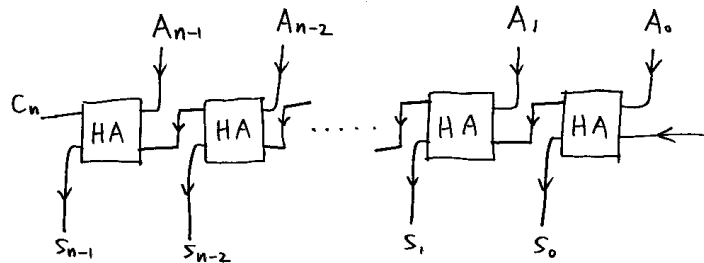

P5.

A) $27_{10} = 1101.1_2 = 1.1011 \times 2^3$.

In IEEE 754 single-precision floating-point format:

0 10000010 101100000000000000000000

Note that in excess-127 representation, the exponent 3 is represented as 10000010. For the mantissa, the leading one is not stored.

B) $10111111\ 00101000\ 00000000\ 00000000 = 1\ 01111110\ 010100000000000000000000$

So the exponent is $126 - 127 = -1$. So the value is

$$-1.0101 \times 2^{-1} = -0.10101_2 = -0.65625_{10}$$

P6. For part A it is straight forward where

$$s_i = (x_i \oplus y_i) \overline{c_i} + \overline{(x_i \oplus y_i)} c_i = x_i \oplus y_i \oplus c_i$$

$$c_i = x_i y_i + x_i c_i + y_i c_i$$

For part B

$$s_i = \overline{x_i} y_i \overline{c_i} + x_i \overline{y_i} \overline{c_i} + \overline{x_i} \overline{y_i} c_i + x_i y_i c_i = (\overline{x_i} y_i + x_i \overline{y_i}) \overline{c_i} + (\overline{x_i} \overline{y_i} + x_i y_i) c_i$$

$$= (x_i \oplus y_i) \overline{c_i} + \overline{(x_i \oplus y_i)} c_i = x_i \oplus y_i \oplus c_i$$

$$c_i = (x_i \oplus y_i) c_i + x_i y_i = (\overline{x_i} y_i + x_i \overline{y_i}) c_i + x_i y_i = y_i (x_i + c_i) + x_i (y_i + c_i) = x_i y_i + x_i c_i + y_i c_i$$

Then A and B expressions are the same. You can also do this exercise with the help of truth tables.

P6.

a. A $2^n \times 1$ multiplexer would take $2^n - 1$ 2×1 multiplexers.

Cpr E 281 HW07 SOLUTION


ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Arithmetic Circuits and Combinational-Circuit Building Blocks

Assigned Date: Eighth Week

Due Date: First class of 9th week

b.

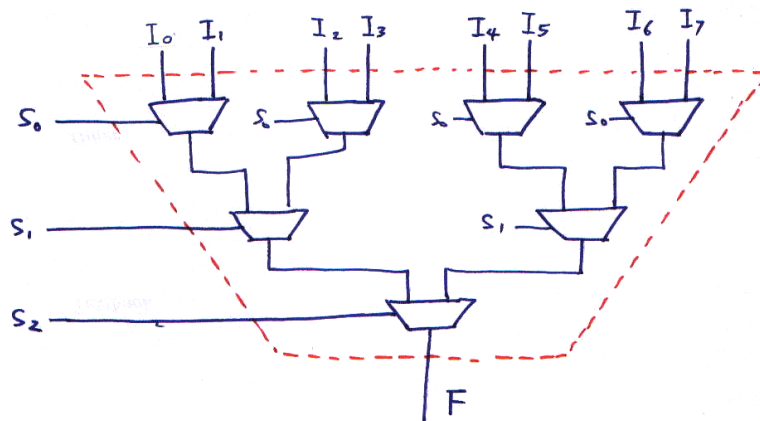

P8. (a)

(a) (b)					(c)
A3	A2	A1	A0	F	
0	0	0	0	1	A0'
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	0
0	1	0	1	0	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	A0
1	0	0	1	1	
1	0	1	0	0	
1	0	1	1	0	
1	1	0	0	1	A0'
1	1	0	1	0	
1	1	1	0	1	
1	1	1	1	1	


(B)

Cpr E 281 HW07 SOLUTION


ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Arithmetic Circuits and Combinational-Circuit Building Blocks

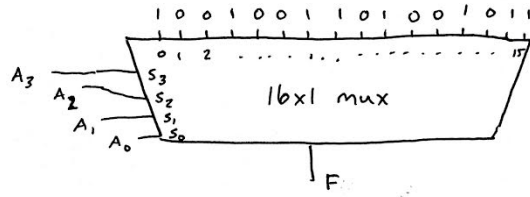Assigned Date: Eighth Week
Due Date: First class of 9th week



(C)

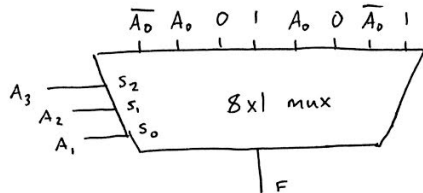

P9.

