
 


P1.

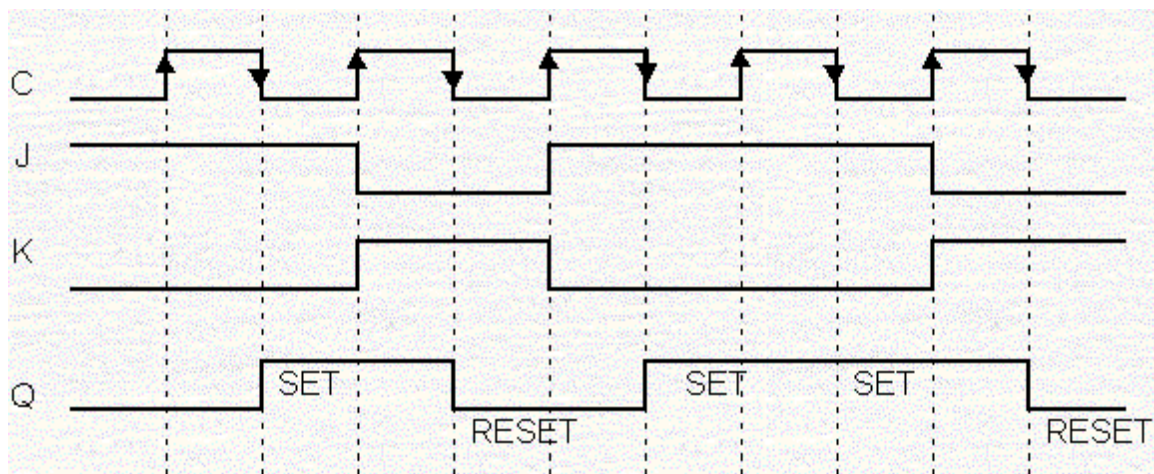

When the Clock is low, the master copies D to Q_m and Q_s is not changed. When the Clock is high, Q_m is not changed and the slave copies Q_m to Q_s . Hence the only time that Q_s ($=Q$) is changed is when the Clock is changing from low to high (i.e., positive clock edge). Then value stored in Q after the positive clock edge is the last value copied from D to Q_m right before the Clock is switched to high.

P2.




P3. This gated D latch design consists of 4 NAND gates and 1 NOT gate.

So total # of transistors in one gated D latch = $4 \times 4 + 1 \times 2 = 18$.

A 64-bit register consists of 128 gated D latches and 64 NOT gates.

Total # of transistors in a 64-bit register = $128 \times 18 + 64 \times 2 = 2432$.

 
P4. We can construct the circuit using four D flip-flops and four 4-to-1 MUXs only.



P5. The counting sequence is 000, 001, 010, 111.

P6. $w=8$, $x=3$, $y=8$, $z=16$, $p=2$, $q=3$, $r=8$

P7.

 

P8.

Solution: let, S_1 select= right shift and S_0 select=left shift

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	W_3	W_2	W_1	W_0
0	1	0	W_3	W_2	W_1
1	0	W_2	W_1	W_0	0
1	1	X	X	X	X

