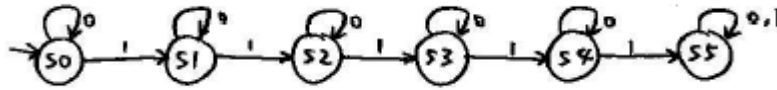


Cpr E 281 HW11 SOLUTION


ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Synchronous Sequential Circuits
Assigned Date: Fourteenth Week
Due Date: First class of 15th week

P1. (a)




(b)

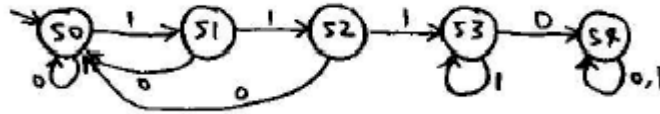

P2.

State transition diagram:

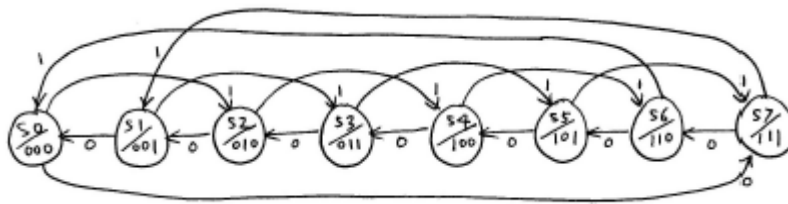

State table with a straightforward state assignment (000 for S0, 001 for S1, etc.):

Present state			Next state						Output		
			w=0			w=1					
y2	y1	y0	Y2	Y1	Y0	Y2	Y1	Y0	z2	z1	z0
0	0	0	1	1	1	0	1	0	0	0	0
0	0	1	0	0	0	0	1	1	0	0	1
0	1	0	0	0	1	1	0	0	0	1	0
0	1	1	0	1	0	1	0	1	0	1	1
1	0	0	0	1	1	1	1	0	1	0	0
1	0	1	1	0	0	1	1	1	1	0	1
1	1	0	1	0	1	0	0	0	1	1	0
1	1	1	1	1	0	0	0	1	1	1	1

The next-state expressions (inputs to D flip-flops) and output expressions are:

$$D_2 = Y_2 = w \bar{y}_2 y_1 + \bar{w} y_2 y_1 + w y_2 \bar{y}_1 + \bar{w} y_2 y_0 + \bar{y}_2 \bar{y}_1 \bar{y}_0 w$$

$$D_1 = Y_1 = w \bar{y}_1 + \bar{y}_1 \bar{y}_0 + \bar{w} y_1 y_0$$

$$D_0 = Y_0 = \bar{y}_0 \bar{w} + y_0 w$$

$$z_2 = y_2$$

$$z_1 = y_1$$

$$z_0 = y_0$$

P3. The state table is:

Present state	Next state		Count
	$w = 0$	$w = 1$	
A	H	C	0
B	A	D	1
C	B	E	2
D	C	F	3
E	D	G	4
F	E	H	5
G	F	A	6
H	G	B	7

The state-assigned table is:

	Present state $y_2 y_1 y_0$	Next state		Output $z_2 z_1 z_0$
		$w = 0$	$w = 1$	
		$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
A	0 0 0	1 1 1	0 1 0	0 0 0
B	0 0 1	0 0 0	0 1 1	0 0 1
C	0 1 0	0 0 1	1 0 0	0 1 0
D	0 1 1	0 1 0	1 0 1	0 1 1
E	1 0 0	0 1 1	1 1 0	1 0 0
F	1 0 1	1 0 0	1 1 1	1 0 1
F	1 1 0	1 0 1	0 0 0	1 1 0
G	1 1 1	1 1 0	0 0 1	1 1 1

The excitation table for T flip-flops is:

Present state $y_2 y_1 y_0$	Flip-flop inputs		Outputs $z_2 z_1 z_0$
	$w = 0$	$w = 1$	
	$T_2 T_1 T_0$	$T_2 T_1 T_0$	
000	111	010	000
001	001	010	001
010	011	110	010
011	001	110	011
100	111	010	100
101	001	010	101
110	011	110	110
111	001	110	111

The expressions for T inputs of the flip-flops are:

$$T_2 = \overline{y_1} \cdot \overline{y_0} \cdot \overline{w} + y_1 \cdot w,$$


$$T_1 = w + \overline{y_0}$$

$$T_0 = \overline{w}$$

The outputs are:

$$z_2 = y_2, z_1 = y_1, z_0 = y_0.$$

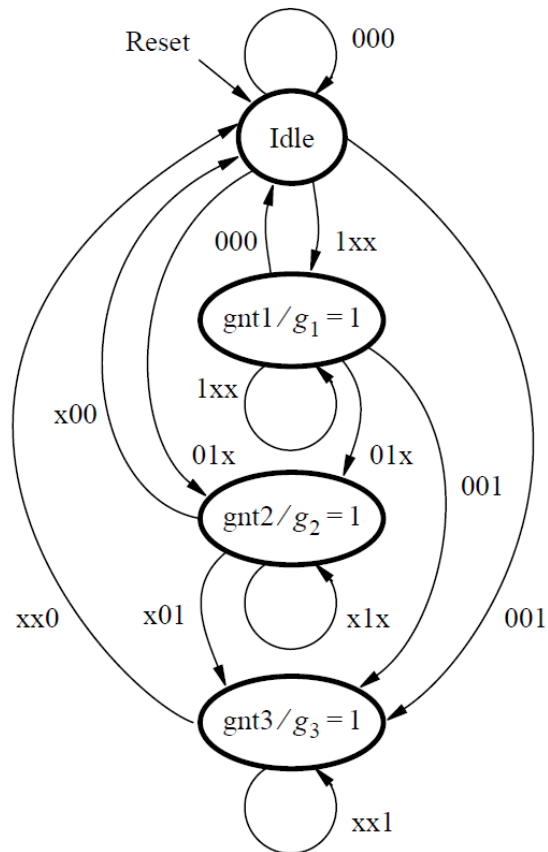P4. To ensure that Device 3 will get serviced the FSM in Figure 6.72 can be modified as follows:



P5. For the state table in Fig. 6.51, using a straightforward state assignment, we have:

	Present state $y_3y_2y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$y_3y_2y_1$	$y_3y_2y_1$	
A	0 0 0	0 0 1	0 1 0	1
B	0 0 1	0 1 1	1 0 1	1
C	0 1 0	1 0 1	1 0 0	0
D	0 1 1	0 0 1	1 1 0	1
E	1 0 0	1 0 1	0 1 0	0
F	1 0 1	1 0 0	0 1 1	0
G	1 1 0	1 0 1	1 1 0	0

$$Y_3 = \bar{w}y_3 + \bar{y}_1y_2 + wy_1\bar{y}_3$$

$$Y_2 = wy_3 + w\bar{y}_1\bar{y}_2 + wy_1y_2 + \bar{w}y_1\bar{y}_2\bar{y}_3$$

$$Y_1 = \bar{y}_3\bar{w} + \bar{y}_1\bar{w} + wy_1\bar{y}_2$$

$$z = y_1\bar{y}_3 + \bar{y}_2\bar{y}_3$$

For the state table in Fig. 6.52, using a straightforward state assignment, we have:

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		y_2y_1	y_2y_1	
A	0 0	0 1	1 0	1
B	0 1	0 0	1 1	1
C	1 0	1 1	1 0	0
F	1 1	1 0	0 0	0

$$Y_2 = \bar{w}y_2 + \bar{y}_1y_2 + w\bar{y}_2$$

$$Y_1 = \bar{y}_1\bar{w} + wy_1\bar{y}_2$$

$$z = \bar{y}_2$$

P6. A minimal state table is

Present state	Next State		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	E	C	0
C	D	C	0
D	A	F	1
E	A	F	0
F	E	C	1

b) An initial attempt at deriving a state table may be

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	D	C	0	0
C	D	C	1	0
D	A	E	0	1
E	D	C	0	0

States B and E are equivalent; hence the minimal state table is

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	D	C	0	0
C	D	C	1	0
D	A	B	0	1