

P1.

(a) Three 2-input ANDs, one 3-input OR.

$$\text{So \# of transistors} = 3 \times 6 + 8 = 26$$

(b) Three NOTs, four 3-input ANDs, one 4-input OR.


$$\text{So \# of transistors} = 3 \times 2 + 4 \times 8 + 10 = 48$$

(c) One NOT, two 2-input ANDs, one 2-input OR.

$$\text{So \# of transistors} = 1 \times 2 + 2 \times 6 + 6 = 20$$


P2.

a)

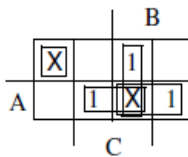


$$F = AB + AC + BC$$

b)

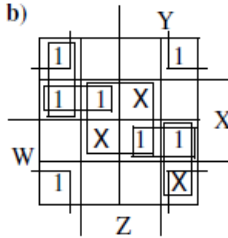

$$F = X'Z' + W'XY' + WXY$$

c)

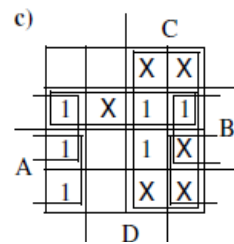

$$F = C + AD' + (BD' \text{ or } A'B)$$

P3. (a) Implement first the complement of f as

$$\begin{aligned} f' &= x1.x3 + x2.x4 \\ &= (x1 \uparrow x3) \uparrow (x2 \uparrow x4) \end{aligned}$$

Then $f = f' \uparrow f'$. Four 2-input NAND gates are used.

(b) Implement first the complement of f as

$$\begin{aligned} f' &= (x1' + x4)(x2' + x3') \\ &= (x1' \downarrow x4) \downarrow (x2' \downarrow x3') \end{aligned}$$


Then $f = f' \downarrow f'$. Four 2-input NOR gates are used.

Cpr E 281 HW05 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

Karnaugh Maps
Assigned Date: Fifth Week
Due Date: First class of 6th week

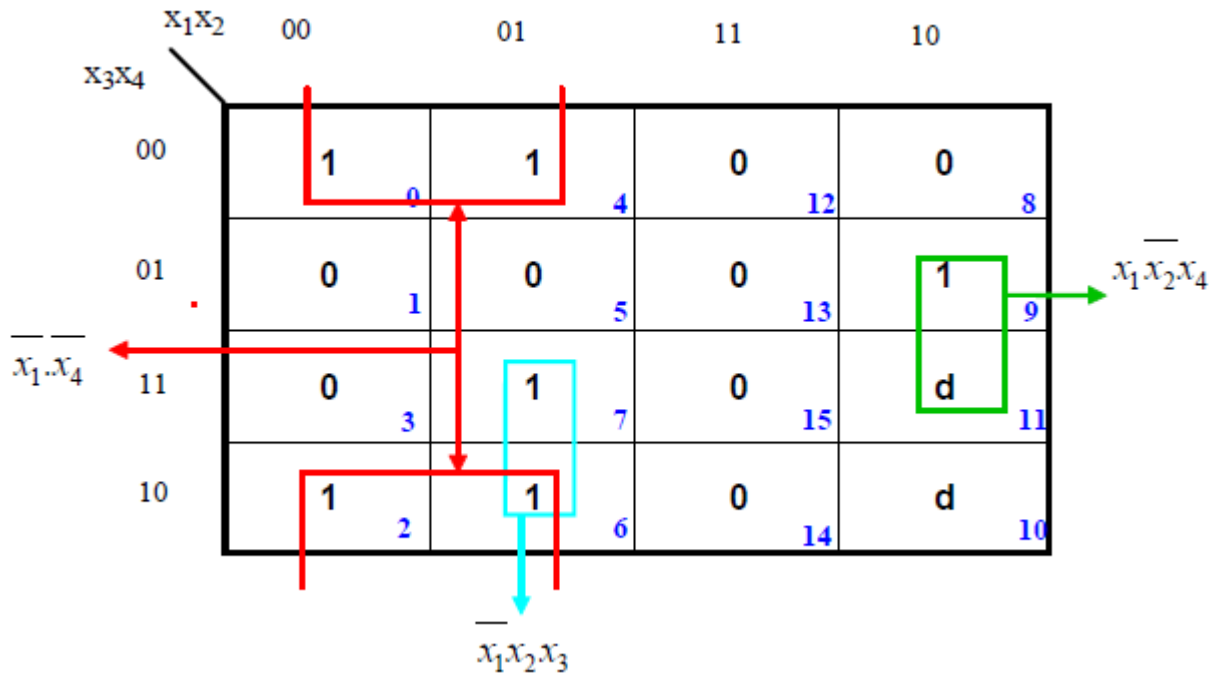P4. The Karnaugh Map for getting the minimum cost SOP form for the function F is:



From the Karnaugh map the minimum cost SOP expression is

$$f(x_1, x_2, x_3, x_4) = \overline{x_1}\overline{x_4} + \overline{x_1}x_2x_3 + \overline{x_1}x_2x_4$$

The realization of function requires,

Two 3-input AND gate.

One 2-input AND gate.

One 3-input OR gate.

The number of gates needed to implementation the function is:


The cost of f = total no. of gates + total no of inputs = $(2+1+1) + \{(2)(3) + (2)(1) + (3)(1)\} = 15$

The Karnaugh Map for getting the minimum cost SOP form for the function G is:

Cpr E 281 HW05 SOLUTION

ELECTRICAL AND COMPUTER
ENGINEERING
IOWA STATE UNIVERSITY

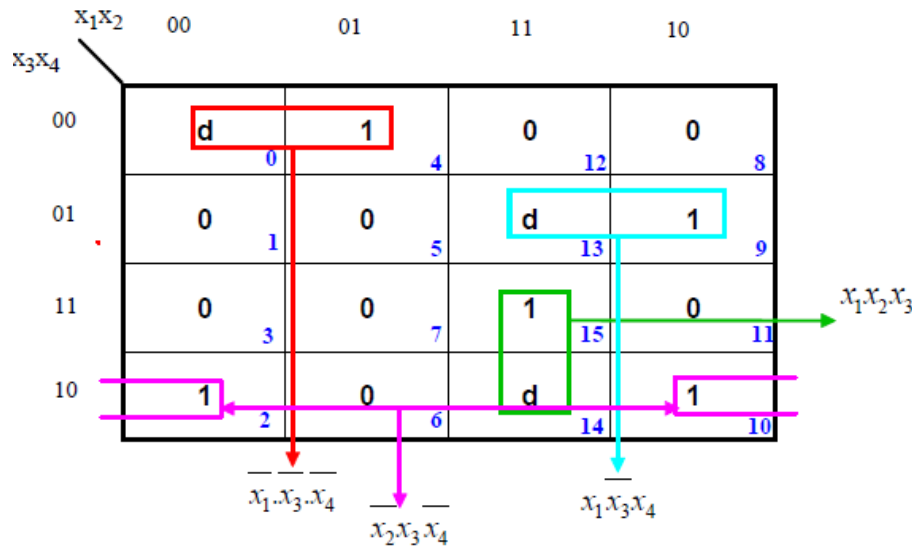Karnaugh Maps
Assigned Date: Fifth Week
Due Date: First class of 6th week



From the Karnaugh map the minimum cost SOP expression is

$$g(x_1, x_2, x_3, x_4) = \overline{x_1} \cdot \overline{x_3} \cdot \overline{x_4} + \overline{x_2} x_3 x_4 + x_1 x_3 x_4 + x_1 x_2 x_3$$

The realization of this function requires,

Four 3-input AND gate.


One 4-input OR gate.

The number of gates needed to implementation the function is:

The cost of g=total no. of gates+ total no of inputs=(4+1)+{(3)(4)+(4)(1)}=21

The total cost of realization of function f and g is=15+21=36

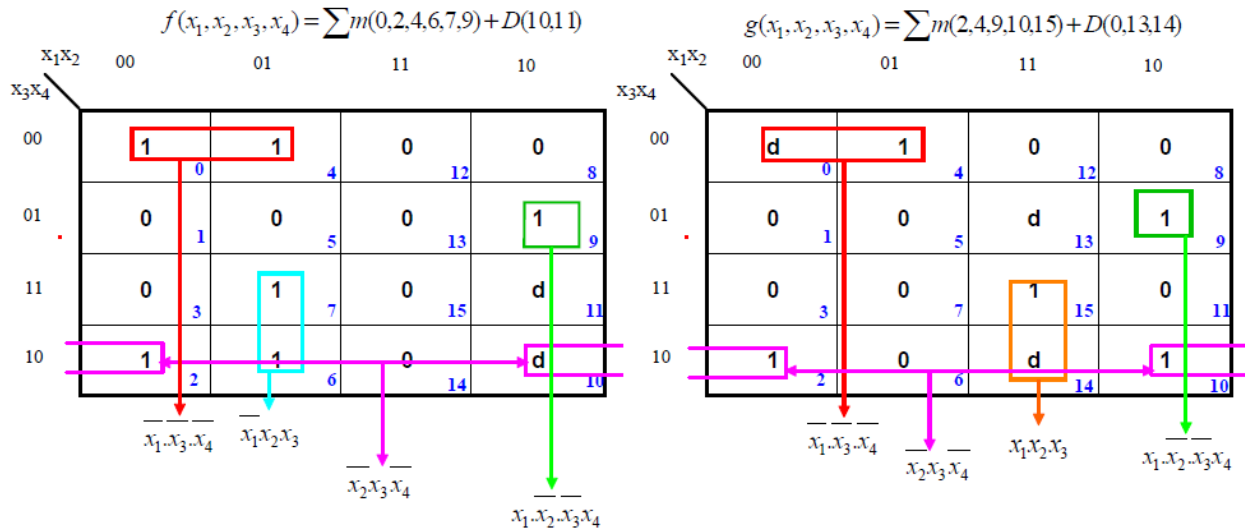In order to find the combined cost of implementing both the function f and g, we draw the Karnaugh map of f and g and groped the elements such that both the function have as many common groping as they possibly can have. Hence the resultant modified Karnaugh maps:



Modified minimum cost SOP forms are

$$f(x_1, x_2, x_3, x_4) = \overline{x_1} \overline{x_3} \overline{x_4} + x_2 x_3 x_4 + x_1 x_2 \overline{x_3} \overline{x_4} + x_1 x_2 x_3$$

$$g(x_1, x_2, x_3, x_4) = \overline{x_1} \overline{x_3} \overline{x_4} + x_2 x_3 x_4 + x_1 x_2 \overline{x_3} \overline{x_4} + x_1 x_2 x_3$$

Hence the first three terms are shared between the two functions.

The implementation of both the functions require:

Four 3-input AND gate

One 4-input AND gate

Two 4-input OR gate

Now the combine cost of the system is

The cost of system = total no. of gates + total no of inputs = $(4+1+2) + \{(3)(4) + (4)(1) + (4)(2)\} = 31$

P5. There are 11 gates and 30 inputs, so the total cost is 41.

After

$$f = \overline{x_1} \overline{x_3} \overline{x_4} + x_1 x_4 + x_3 x_4 + \overline{x_1} \overline{x_2} x_3 + x_1 x_2 \overline{x_3} \overline{x_4}$$

$$g = \overline{x_1} \overline{x_4} + \overline{x_1} x_3 + x_3 \overline{x_4} + \overline{x_2} x_4 + x_1 x_2 \overline{x_3} \overline{x_4}$$

K-map of f, g shows below:

		X1 X2			
X3X4		00	01	11	10
00	(1)	1	1	0	
01	0	0	1	1	
11	1	1	1	1	
10	(1)	0	0	0	

		X1 X2			
X3X4		00	01	11	10
00	(1)	1	1	0	
01	1	0	0	1	
11	1	1	0	1	
10	(1)	1	1	1	

Then based on the optimum combined circuit:

$$f = x_2 \bar{x}_3 \bar{x}_4 + \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_3 x_4 + x_1 x_4$$

$$g = x_2 \bar{x}_3 \bar{x}_4 + \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_3 x_4 + \bar{x}_2 x_4 + x_3 \bar{x}_4$$

So f and g share the first three product terms.

The cost 8 gates, 24 inputs. Total cost of redesigned solution: 32.

Note that other solutions are possible depending on which 1's combination are taken (but they must have at least 3 common factors in k-maps for f and g expressions)

P6. The SOP joint minimization:

$$F = W + X \bar{Y} + X \bar{Z} + \bar{Y} \bar{Z}$$

$$G = W + X \bar{Y} + X \bar{Z} + \bar{X} Y$$

Note that the POS joint minimization has the same cost of 22:

$$F = (\bar{X} + \bar{Y} + \bar{Z})(W + X + \bar{Z})(X + \bar{Y})$$

$$G = (\bar{X} + \bar{Y} + \bar{Z})(W + X + Y)$$